
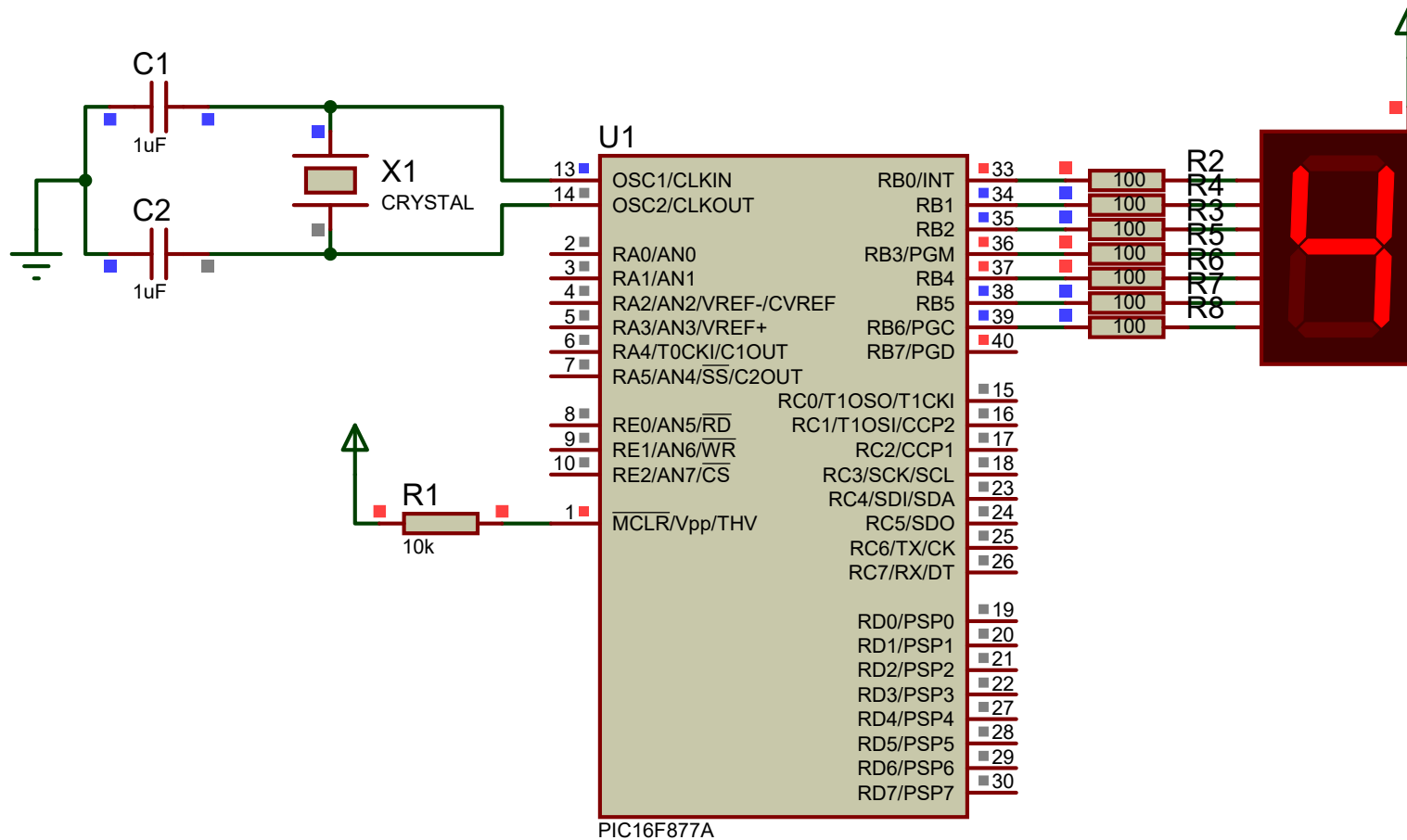



**Figure: Interfacing the LED blinking using PIC16F877A**

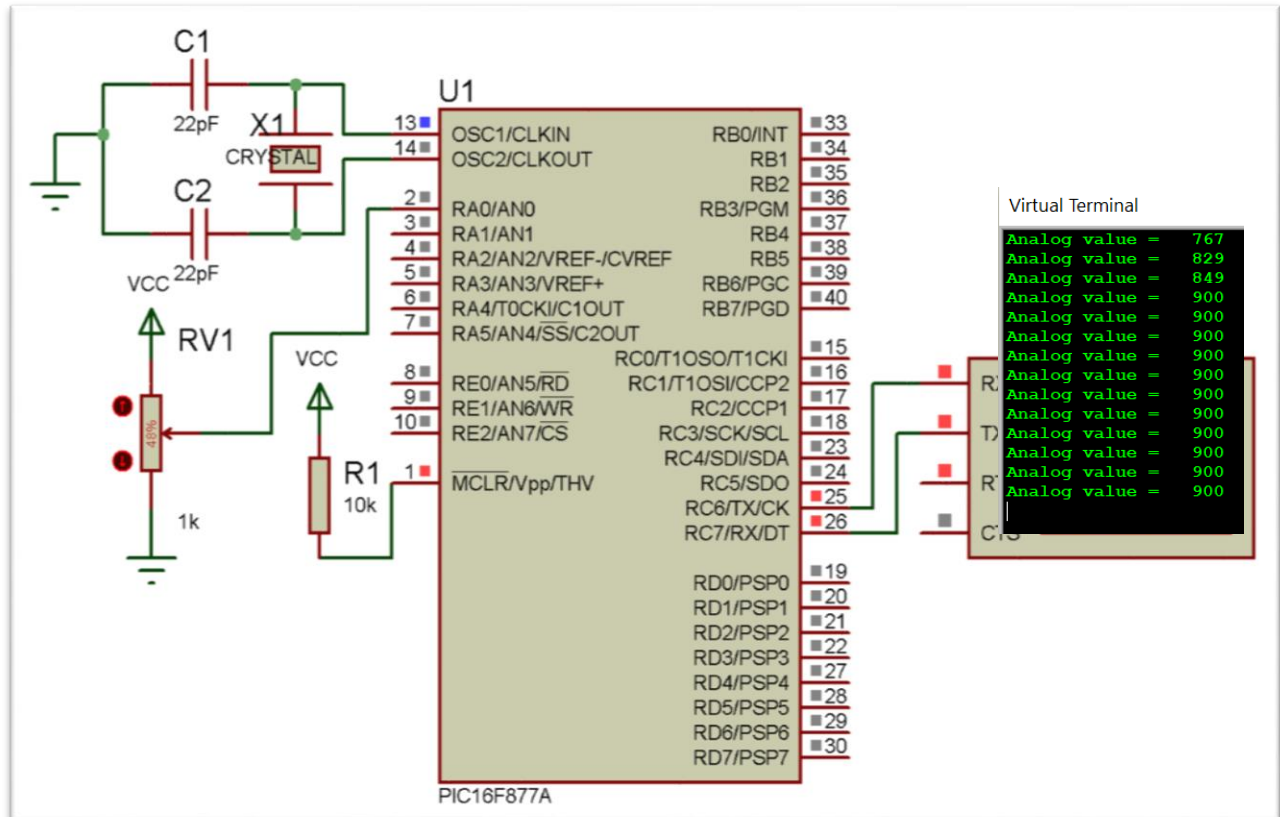


**Figure: Interfacing the 7 segment LED display using PIC16F877A microcontroller**




**Figure: Reading the ADC value in virtual terminal using PIC16F877A**

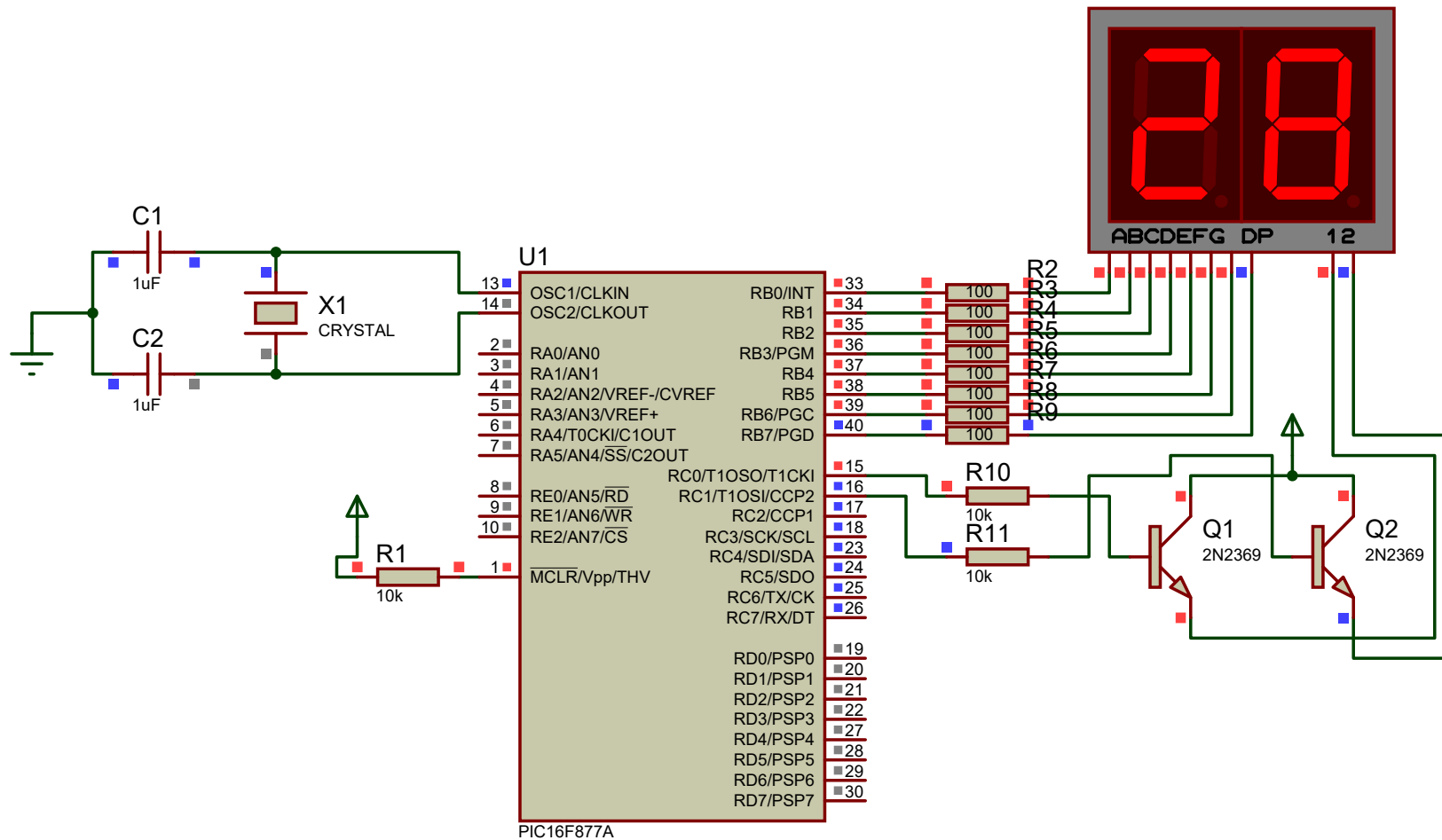


**Figure: Multiplexing of 7 segment LED display using PIC16F877A Microcontroller.**

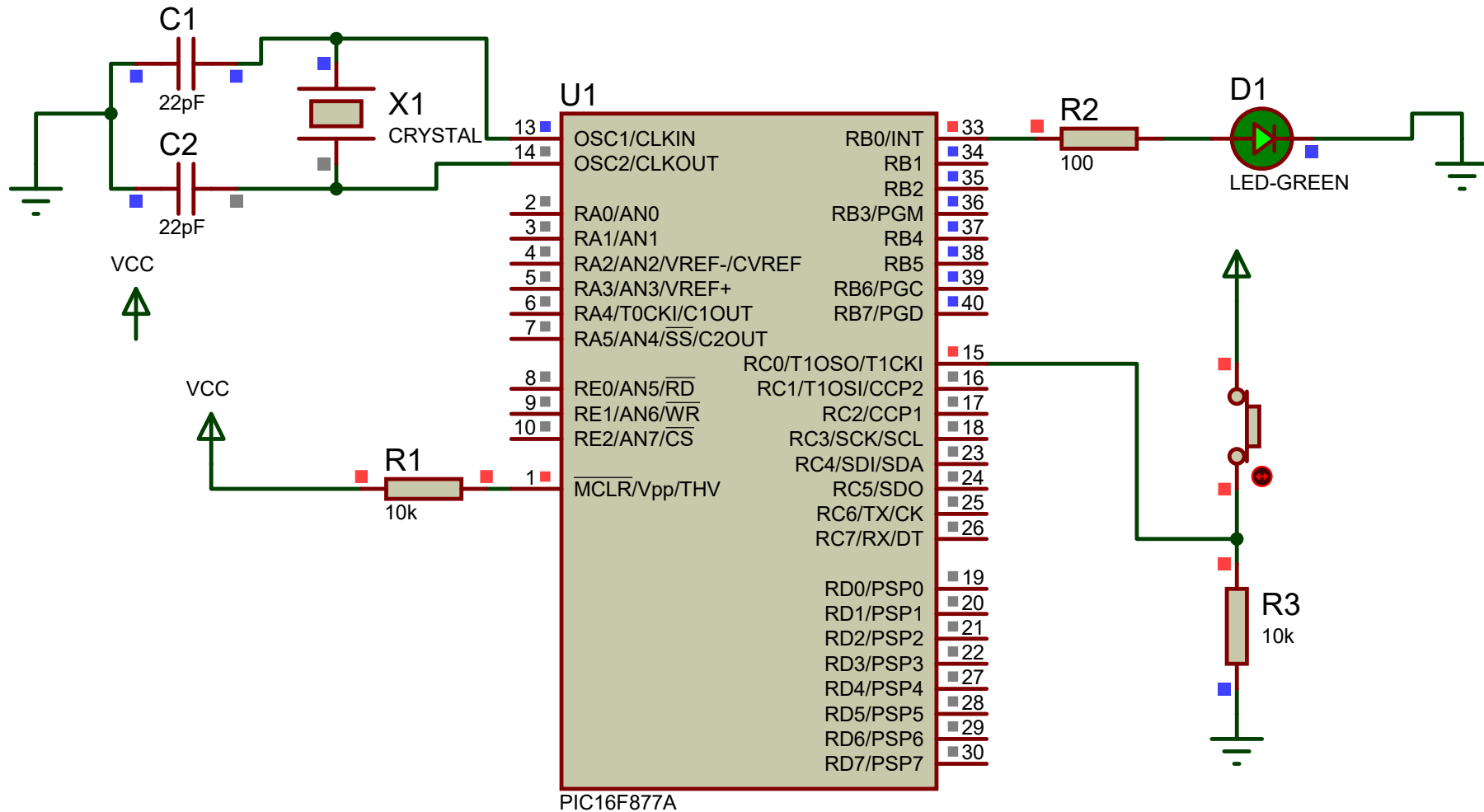


**Figure: Interfacing the LED with push button using PIC16F877A microcontroller**

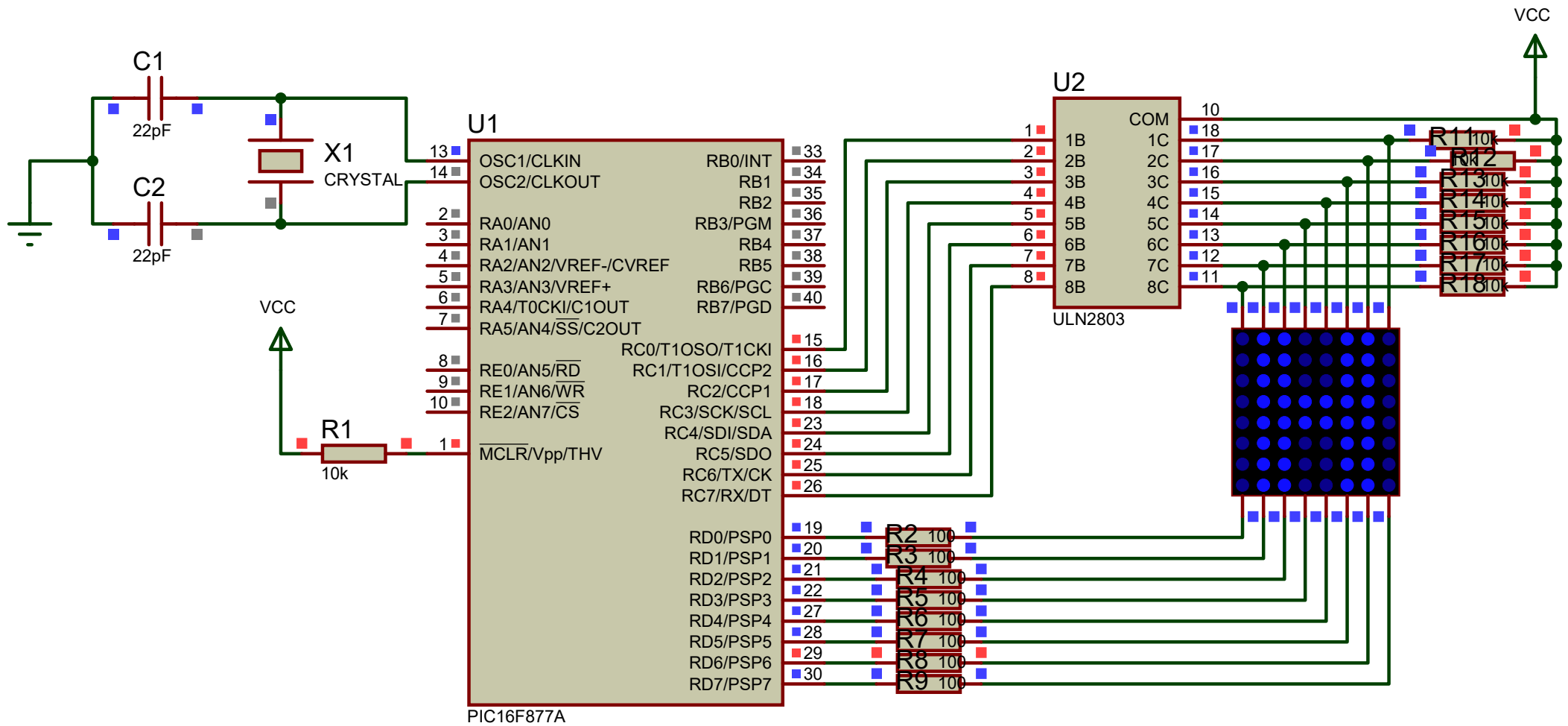

**Figure: Interfacing the Dot matrix using PIC16F877A**

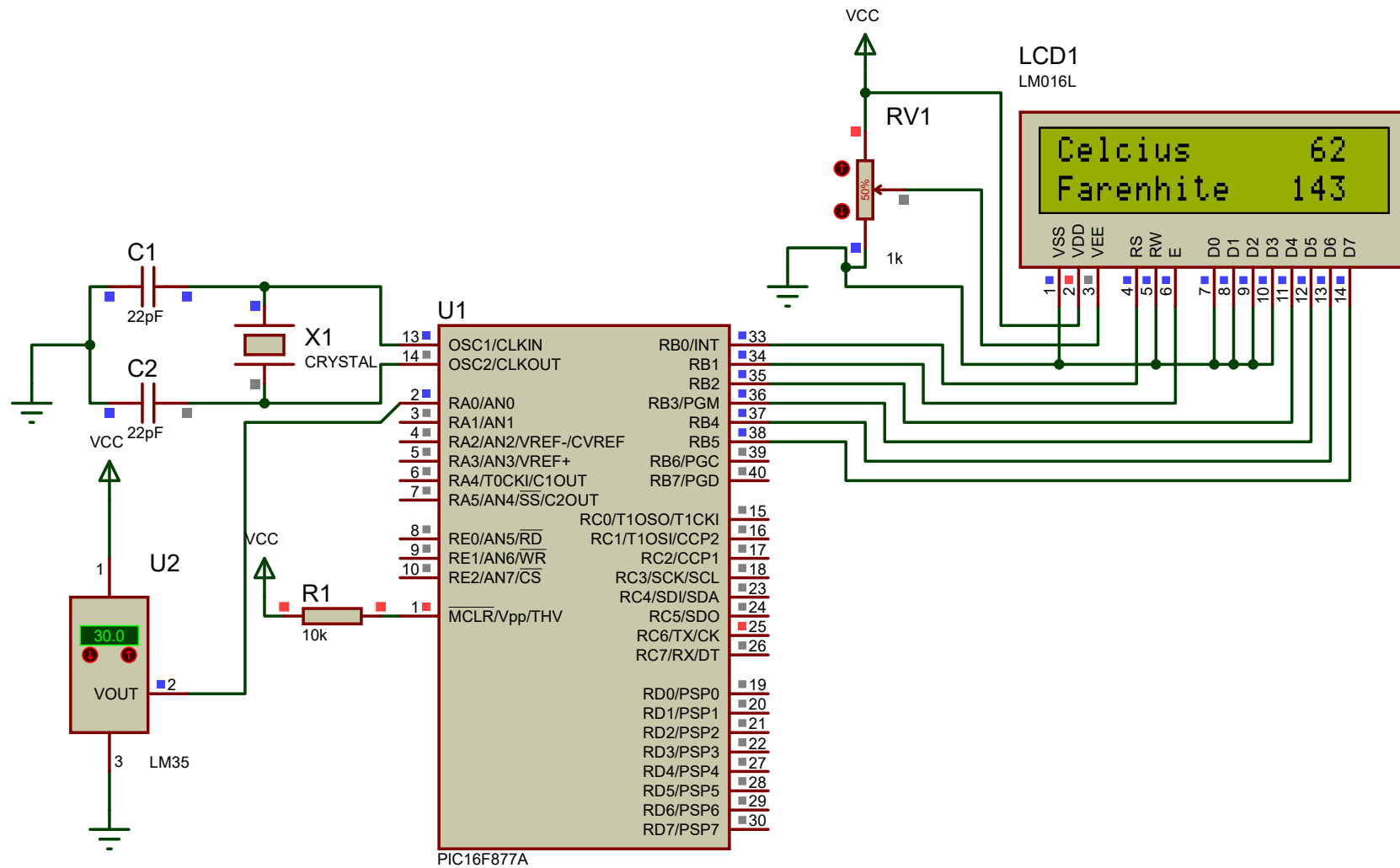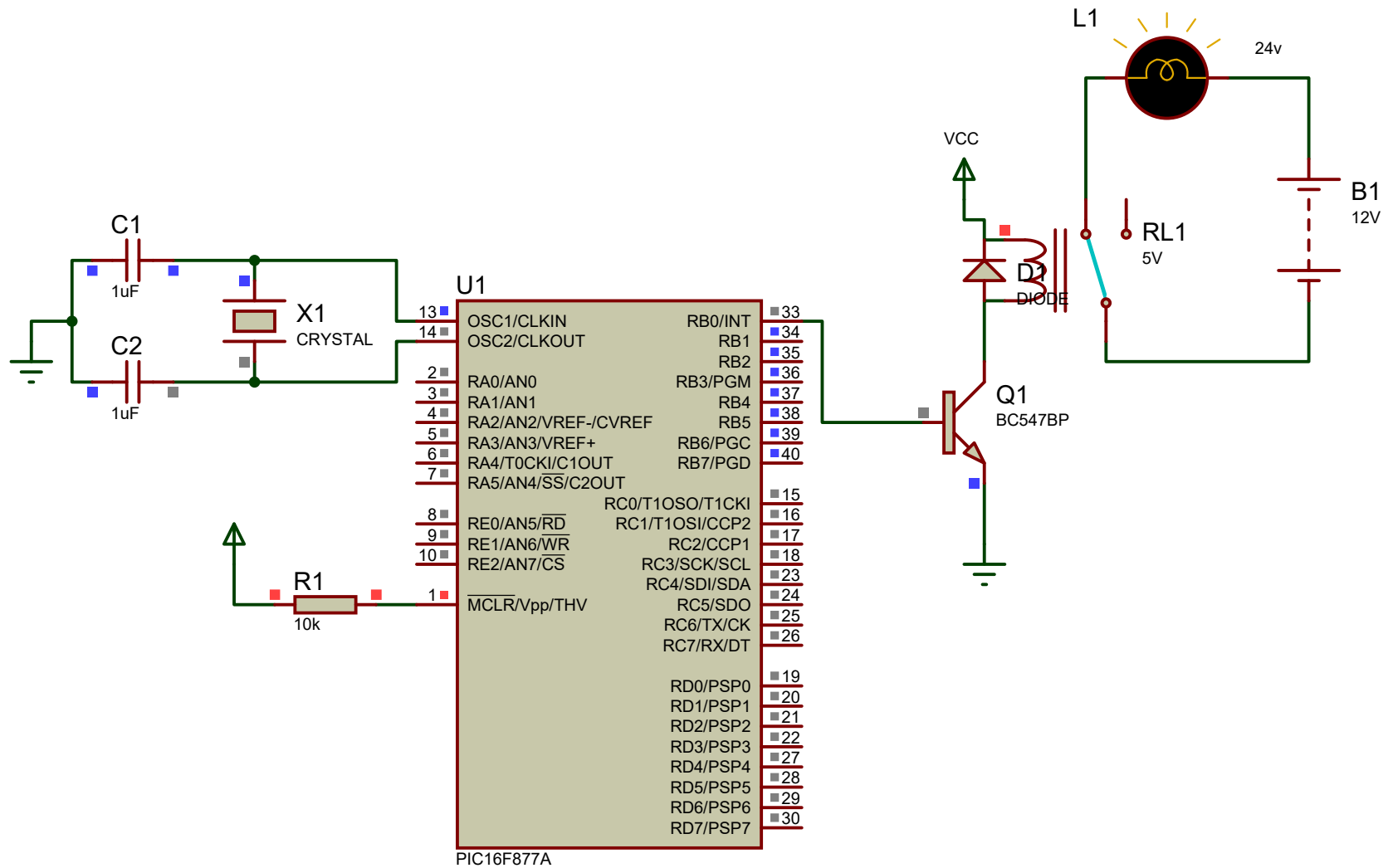


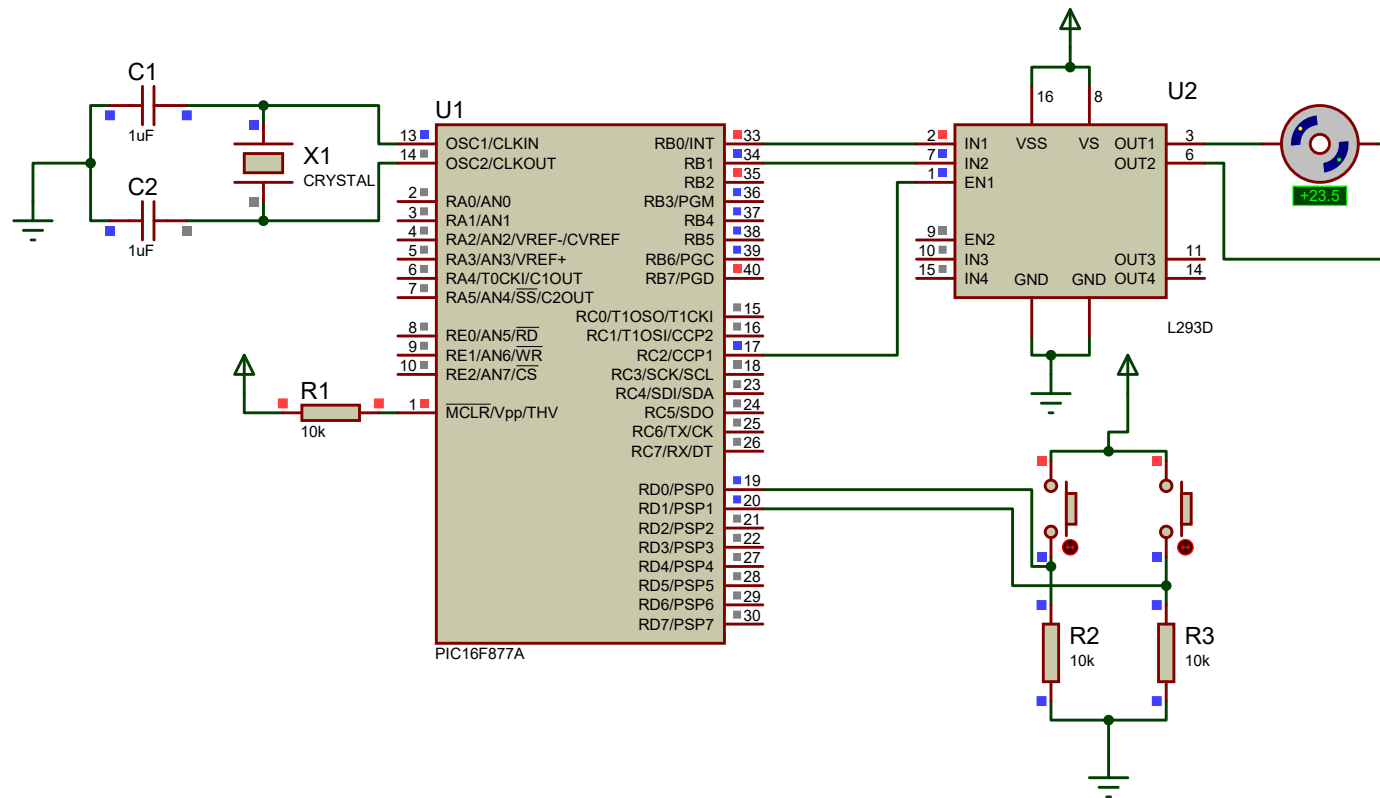**Interfacing the LM-35 temperature sensor using pic16F877A microcontroller**

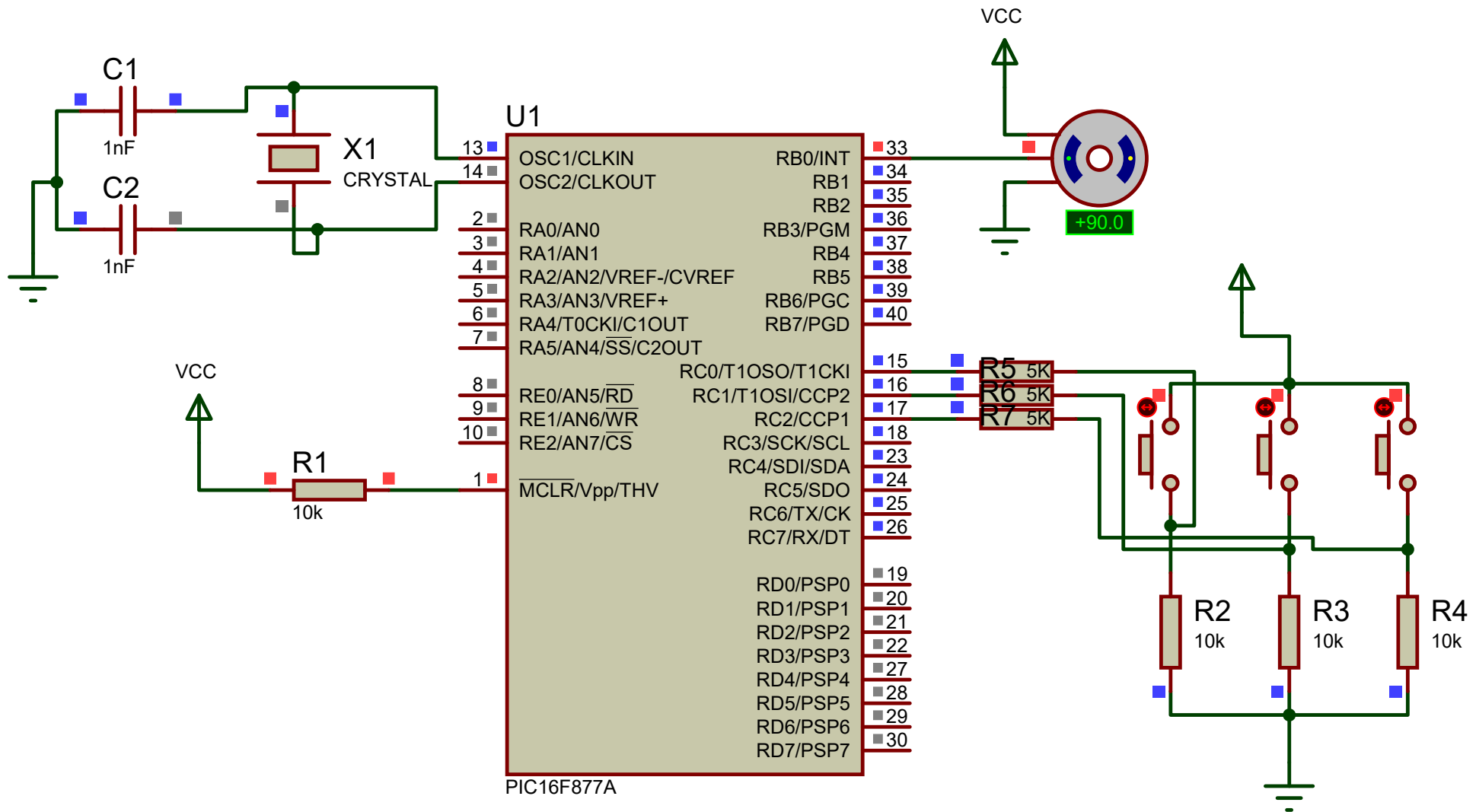


**Figure: Interfacing the relay with PIC16F877A Microcontroller.**

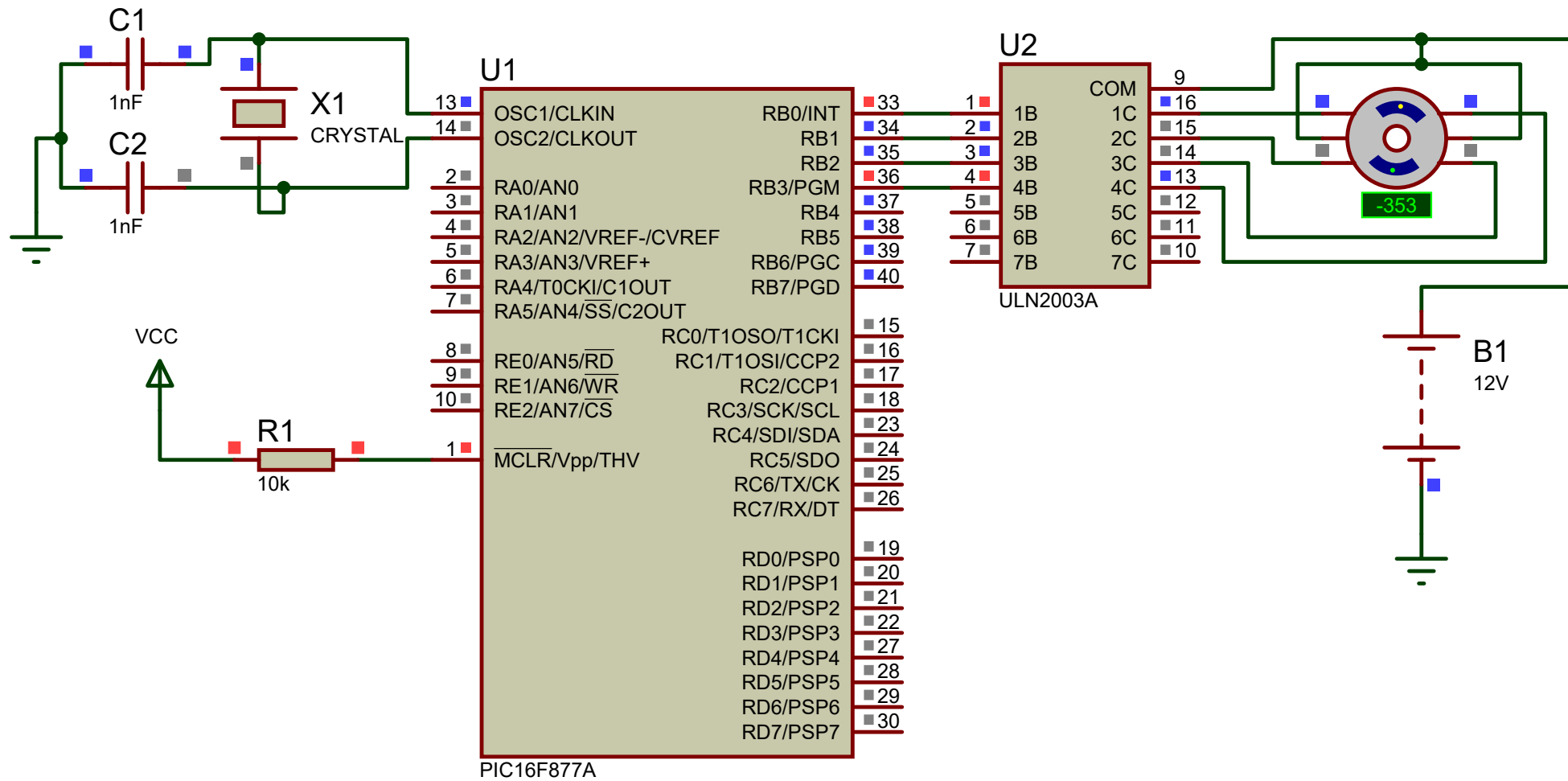




**Figure: Interfacing PWM and speed control of DC motor with PIC16F877A Microcontroller.**



**Figure: Interfacing servo using PIC16F877A**



**Figure: Interfacing the stepper motor using PIC16F877A**